

PROJECT REPORT

32-Bit 5-Stage Pipelined MIPS Processor

(Phase 1: RTL Architecture)

Author: Mina S. ElHanash

Junior, Electronic and Communication Engineering

Institution: Ain Shams University, Faculty of Engineering

Date: February 2026

Table of Contents

ABSTRACT	4
1.0 INTRODUCTION	5
1.1 Background on MIPS Architecture	5
1.2 Project Objectives	6
2.0 PROJECT SPECIFICATIONS.....	7
3.0 DESIGN METHODOLOGY	10
3.1 Phase 1 of the Design: Single-Cycle Architecture Validation	10
3.1.1 Program counter (pc) next-state logic expansion	10
3.1.2 Decoupled data memory addressing	11
3.1.3 Extended register file destination routing	12
3.2 Phase 2: Pipelined Architecture and Hazard Management.....	13
4.0 VERILOG CODES AND MODULE HIERARCHY	14
4.1 Program Counter	14
4.2 MUX 2x1 32-Bits	15
4.3 Instruction Memory	16
4.4 Adder	17
4.5 IF ID Stage Register	18
4.6 Register File	19
4.7 Sign Extender	20
4.8 Control Unit	21
4.9 Hazard Detection Unit	23
4.10 ID EX Stage Register.....	24
4.11 ALU	28
4.12 ALU Control Unit	29
4.13 MUX 4x1 32-Bits	30
4.14 MUX 4x1 5-Bits	30
4.15 Forwarding Unit.....	31
4.16 EX MEM Stage Register	32

4.17 Data Memory	36
4.18 MEM WB Stage Register	37
4.19 Top Module	39
5.0 SYNTHESIS AND IMPLEMENTATION	51
6.0 CONCLUSION	56

ABSTRACT

This report details the Phase 1 design, synthesis, and implementation of a 32-bit, 5-stage pipelined MIPS processor. The core was developed using Verilog HDL with a focus on structural microarchitecture, incorporating full hazard detection and data forwarding to resolve Read-After-Write (RAW) and control hazards. The design was synthesized using Xilinx Vivado targeting a Spartan-7 FPGA (xc7s50csga324-1). Post-implementation timing analysis confirms the processor successfully meets a 100 MHz clock constraint, achieving a Maximum Clock Frequency (Fmax) of 105.7 MHz. This completed RTL architecture establishes the foundation for Phase 2, which will focus on functional verification using SystemVerilog and the Universal Verification Methodology (UVM).

1.0 INTRODUCTION

1.1 Background on MIPS Architecture

The MIPS (Microprocessor without Interlocked Pipelined Stages) architecture is a cornerstone of modern digital design, widely recognized as one of the most elegant implementations of Reduced Instruction Set Computer (RISC) principles. Developed in the early 1980s, the MIPS ISA was designed with a strict load/store architecture, meaning all arithmetic and logical operations are performed exclusively on data held within the processor's internal registers, while memory is accessed solely through dedicated load and store instructions. This deliberate simplicity, combined with a fixed 32-bit instruction length, allows the hardware to decode and execute instructions with high efficiency.

To maximize instruction throughput, the MIPS architecture inherently supports pipelining. By dividing instruction execution into five distinct, sequential stages-Instruction Fetch (IF), Instruction Decode (ID), Execute (EX), Memory Access (MEM), and Write Back (WB)-the processor can process multiple instructions concurrently. While pipelining dramatically increases the theoretical execution rate by ensuring the CPU completes one instruction per clock cycle under ideal conditions, it introduces significant microarchitectural challenges known as hazards.

Hazards occur when the pipeline must be stalled to prevent incorrect execution. **Structural hazards** arise from hardware resource conflicts, **data hazards** (such as Read-After-Write) occur when an instruction depends on the result of a preceding, uncompleted instruction, and **control hazards** are caused by branch instructions altering the flow of the program counter. A sophisticated MIPS implementation must move beyond basic interlocked stalling and incorporate dynamic hardware solutions, such as data forwarding and branch prediction, to maintain pipeline efficiency.

1.2 Project Objectives

The primary objective of this project is to architect, synthesize, and validate a fully functional 32-bit, 5-stage pipelined MIPS processor at the Register Transfer Level (RTL). Rather than relying on high-level behavioral modeling, this project focuses on structural, synthesizable microarchitecture, serving as a comprehensive exercise in digital logic design and physical hardware implementation.

The specific objectives of Phase 1 include:

- **Gate-Level RTL Implementation:** To develop a complete Verilog HDL codebase that accurately models the MIPS data path and control logic, strictly adhering to synthesizable coding guidelines.
- **Dynamic Hazard Resolution:** To implement an active Forwarding Unit capable of bypassing the register file to resolve Read-After-Write (RAW) data hazards dynamically. Additionally, to construct a Hazard Detection Unit that injects hardware bubbles (stalls) only when data forwarding is mathematically insufficient, such as during Load-Use hazards.
- **Physical Synthesis and Benchmarking:** To move the design beyond idealized software simulation by targeting a modern Xilinx Spartan-7 FPGA (xc7s50csga324-1). This includes analyzing the physical mapping of logic gates to extract real-world hardware utilization metrics (Slice LUTs and Registers) and performing static timing analysis to verify the processor achieves a minimum Maximum Clock Frequency (Fmax) of 100 MHz.
- **Establishing a Verification Baseline:** To create a mathematically sound and physically proven RTL core (Phase 1) that will serve as the Design Under Test (DUT) for Phase 2. The ultimate objective of this multi-phase project is to subject this synthesizable core to rigorous functional verification using SystemVerilog and the Universal Verification Methodology (UVM) to achieve complete code and functional coverage.

2.0 PROJECT SPECIFICATIONS

Course Project (Major Task)

Fall 2025

Aim

This project aims to design, simulate, and synthesize a modified single-cycle and pipelined RISC-style processor in Verilog on an FPGA that supports a subset of the RISC instruction set. The project includes the architecture form, where the students will focus on developing a tailored architecture to perform a specific function.

The *processor* should support:

- the arithmetic and logic operations: **add, sub, and, or, andi, addi, slt**
- Memory-reference: **lw, sw**
- jumping and branching: **j, beq**
- In addition to three new instructions: **jmn, swi, PMC**

where the format and description of each instruction is as follows:

	6-Bits	5-Bits	5-Bits	5-Bits	5-Bits	6-Bits
I-type	op	rs	rt	immediate		
J-type	op	---	address			
R-type	op	rs	rt	rd	---	func

pmc (rt), imm(rs)	# Perform two operations: ➤ PC = Memory[R[rt]] ; set the value of PC to the loaded data from memory location Memory[R[rt]] ➤ Memory[R[rs] + imm] = PC + 4 ; store the new value of PC to a memory location Memory[R[rs] + imm]
jmn imm(rs)	#Indirect Jump. PC = Memory[imm + R[rs]] , I-format instruction will cause the processor to jump to the address stored in the word at memory location imm + R[rs] .
swi rt, imm(rs)	#I-format instruction will perform two operations: ➤ it stores the contents of R[rt] at the memory address (R[rs] + imm) then, increments R[rs] by the immediate imm .

Phase 1 — ALU & Register File

Design and implement the ALU and register file:

- ALU ops: add, sub, and, or, andi, addi, slt, maybe logical immediates.
- Register file: 32×32 registers, two read ports, one write port, synchronous write, async read.

Deliverables

- RTL code (fully commented)
- Testbench and waveform screenshots

Phase 2 — Single-Cycle Processor

Integrate ALU and register file into a single-cycle CPU (fetch → decode → execute → mem → writeback) that executes the proposed instruction subset.

Specs

- Minimal ISA mentioned above.
- Memories: instruction memory (initial content from assembled test programs), data RAM (read/write).

Verification

- Use assembly test programs saved in Imem or load from a hex file.
- Check expected memory and register states after program execution.
- Create self-checking testbenches that compare expected registers/memory.

Synthesis

- Run the CAD tool to produce a flattened gate netlist.

Deliverables

- Single-cycle RTL + testbenches, simulation traces, synthesized netlist.
- Synthesis and timing reports describing datapath and control signals.

Phase 3 — Pipelined Processor

Convert a single-cycle CPU into a 5-stage pipelined CPU: IF, ID, EX, MEM, WB.

Architecture

- Add pipeline registers between stages and Split control and datapath accordingly
- Manage instruction fetch PC update, branch resolution (choose branch in EX or ID — pick one and document)

Verification & Simulation

- Use longer assembly test programs that reveal hazards (e.g., dependent instruction sequences)
- Create a self-checking harness that runs for N cycles and compares the final register/memory content.

Synthesis

- Synthesize pipeline; check timing reports using FPGA flow

Deliverables

- RTL with pipeline registers, test programs that show pipeline behavior, simulation waveforms
- Proof of correct output despite pipeline (before hazard handling)
- Synthesis and timing reports describing datapath and control signals.

Phase 4 — Hazard Detection & Forwarding (Stalling & Bypass)

Implement the hazard detection unit (HDU) and forwarding (bypass) unit to eliminate or reduce stalls caused by data hazards; implement control for load-use stall.

Verification

- Write specific test programs with sequences requiring forwarding and load-use:
 - e.g., ADD R1, R2, R3 followed by SUB R4, R1, R5 (forwarding from EX)
 - LW R1, 0(R2) followed by ADD R3, R1, R4 (load-use: one cycle stall required)
- Self-checking testbenches verify register contents at known cycle counts
- Provide waveforms showing forwarding mux selection and inserted bubble
- **Corner cases**
 - Multi-cycle memory/IO (if implemented)
 - Branch + load interactions
 - Structural hazards if you reuse memory ports — avoid by design or document

Deliverables

- Hazard and forwarding RTL, testbenches with annotated waveforms, final reports describing the algorithm, synthesis and verification

 


Figure 2: Added pmc MUX.

3.1.2 Decoupled data memory addressing

The standard memory interface was restructured to decouple the read and write address computations. In a traditional MIPS architecture, the ALU result strictly dictates the memory address. To support custom instructions, dedicated multiplexers were introduced at the address ports. The read address can now be dynamically sourced from either the ALU result or directly from the second register operand (Read Data 2). Concurrently, the write address can be sourced from the ALU result or the PC+4 path. This allows the architecture to execute custom operations, such as pushing the current program counter directly into memory or performing register-direct memory accesses without routing through the ALU.

 


Figure 3: Dual port data memory with 2 MUXs to select the read address and the write data.

3.1.3 Extended register file destination routing

The write-back stage logic was modified by upgrading the standard 2-to-1 write destination multiplexer into a 3-to-1 multiplexer. While traditional MIPS limits the destination register to either the *rt* field (instruction[20:16]) for I-type or the *rd* field (instruction[15:11]) for R-type instructions, this architectural change introduces a third selection path. It allows the *rs* field (instruction[25:21]) to act as the write destination. This modification specifically accommodates custom instructions designed to compute a result and directly overwrite the first source register.

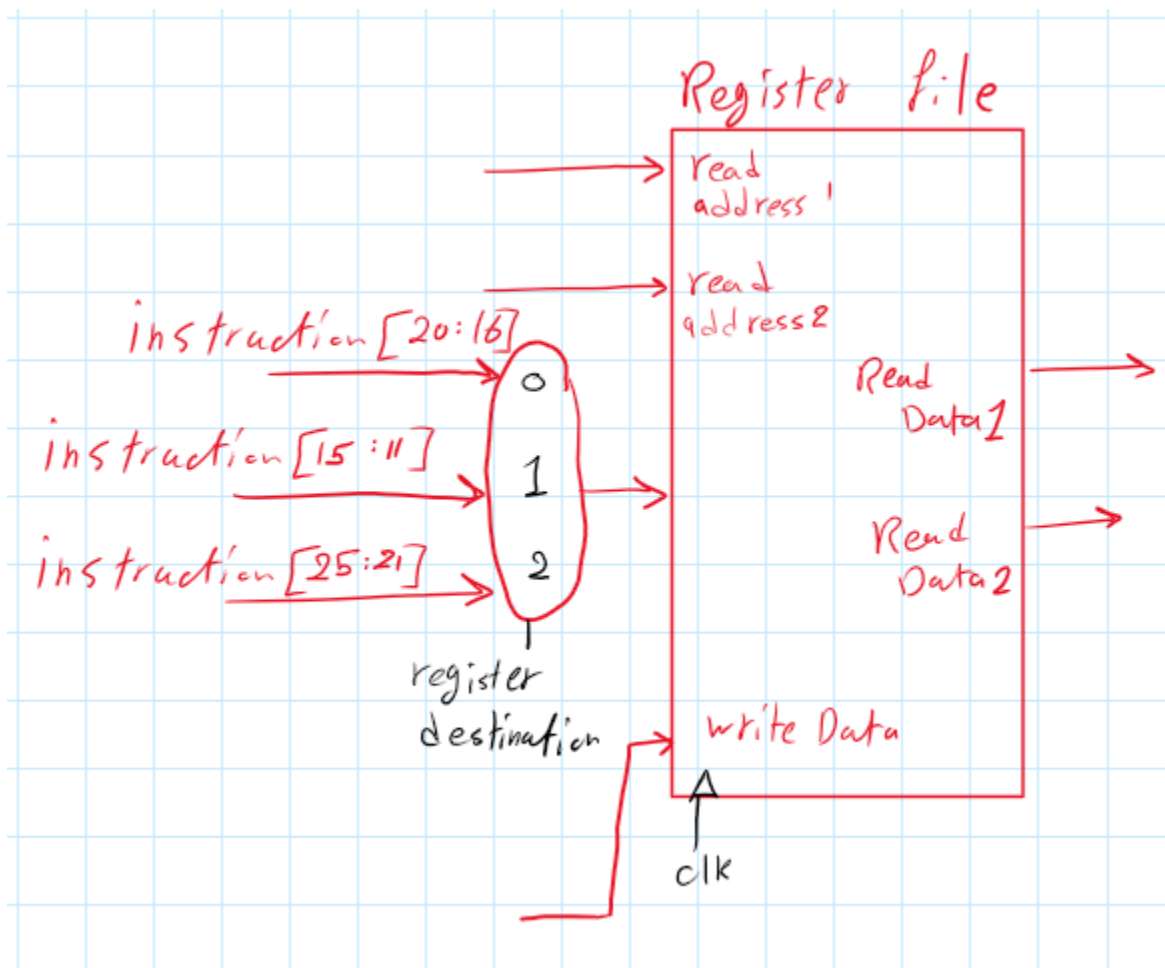


Figure 4: Expanded write address MUX.

3.2 Phase 2: Pipelined Architecture and Hazard Management

Following the validation of the single-cycle core, the architecture was partitioned and upgraded into a high-performance 5-stage pipelined design. To maintain data integrity across concurrent instruction executions, the following structural components were integrated:

- **Data Path:** Registers separate each of the five pipeline stages (IF/ID, ID/EX, EX/MEM, MEM/WB) to hold intermediate calculations and control signals.
- **Control Unit:** A hardwired main control unit decodes the 6-bit opcode in the ID stage and propagates the control signals through the pipeline registers to the EX, MEM, and WB stages.
- **Forwarding Unit:** To prevent stalling during RAW hazards, the forwarding unit monitors the destination registers of instructions in the EX/MEM and MEM/WB stages. If a dependent instruction enters the EX stage, the multiplexers bypass the Register File and forward the computed data directly to the ALU inputs.
- **Hazard Detection Unit:** If a Load-Use hazard occurs (e.g., an LW instruction followed immediately by an instruction that needs the loaded data), forwarding alone is insufficient. The Hazard Detection unit freezes the PC and IF/ID registers and flushes the ID/EX register (inserting a hardware bubble) for one clock cycle.

 


Figure 5: MIPS Pipeline CPU Architecture [2].

4.0 VERILOG CODES AND MODULE HIERARCHY

4.1 Program Counter

```
program_counter.v
1  module program_counter (
2      input [31:0] next_pc,
3      input rst, clk, overflow_flag, write_enable,
4      output reg [31:0] current_pc
5  );
6
7      always @(posedge clk or posedge rst) // asynchronous reset, PC will reset regardless of th clk
8      begin
9          if (rst)
10             begin
11                 current_pc <= 32'd0;
12             end
13             else if (overflow_flag)
14                 begin
15                     current_pc <= current_pc;
16                 end
17             else if (write_enable) begin
18                 current_pc <= next_pc;
19             end
20             else
21                 begin
22                     current_pc <= current_pc;
23                 end
24             end
25
26  endmodule
```

4.2 MUX 2x1 32-Bits

```
≡ mux_2to1_32bits.v
1  module mux_2to1_32bits (
2      input [31:0] input_1, input_2,
3      input select,
4      output [31:0] mux_out
5  );
6
7      assign mux_out = select?input_2:input_1;
8
9  endmodule
```

4.3 Instruction Memory

≡ instruction_memory.v

```
1  module instruction_memory (  
2      input [31:0] pc,  
3      output [31:0] instruction  
4  );  
5      wire [31:0] pc_by_4; // as address 1 in instruction memory is equal to "pc = 4"  
6      // in other words, MIPS is byte aligned and each word is 4 bytes  
7  
8      reg [31:0] instruction_memory_registers [0:255];  
9  
10     assign pc_by_4 = pc >> 2;  
11     assign instruction = instruction_memory_registers [pc_by_4];  
12  
13     initial // load "instructions.hex" into the instruction memory  
14     begin  
15         $readmemh("instructions.hex", instruction_memory_registers );  
16     end  
17  
18 endmodule
```


4.4 Adder

```
adder.v
1  module adder (
2      input [31:0] input_1, input_2,
3      output [31:0] adder_output
4  );
5
6      assign adder_output = input_1 + input_2;
7
8  endmodule
```

4.5 IF ID Stage Register

```
if_id_stage.v
1  module if_id_stage (
2      input clk, rst,
3      input write_enable, flush,
4      input [31:0] instruction_in, pc_in, pc_plus_4_in,
5      output reg [31:0] instruction_out, pc_out, pc_plus_4_out
6  );
7
8      always @(posedge clk or posedge rst) begin
9          if (rst) begin
10             instruction_out <= 32'd0;
11             pc_plus_4_out <= 32'd0;
12             pc_out <= 32'd0;
13         end
14         else if (flush) begin
15             instruction_out <= 32'd0;
16             pc_plus_4_out <= 32'd0;
17             pc_out <= 32'd0;
18         end
19         else if (write_enable) begin
20             instruction_out <= instruction_in;
21             pc_plus_4_out <= pc_plus_4_in;
22             pc_out <= pc_in;
23         end
24         else begin
25             instruction_out <= instruction_out;
26             pc_plus_4_out <= pc_plus_4_out;
27             pc_out <= pc_out;
28         end
29     end
30
31 endmodule
```

4.6 Register File

≡ register_file.v

```
1  module register_file (
2      input [4:0] read_address_1, read_address_2, write_address,
3      input [31:0] write_data,
4      input reg_write, clk, rst,
5      output [31:0] reg_out_1, reg_out_2
6  );
7      reg [31:0] registers [0:31]; // 32 register each with width of 32 bit
8      integer i; // used in the for loop for clearing the content of the registers
9
10
11     always @(posedge clk)
12     begin
13         if (rst) // reset the content of all register to zero
14         begin
15             for (i = 1 ; i<32 ; i = i+1 ) begin
16                 registers[i] <= 32'd0;
17             end
18         end
19         else if (reg_write && (write_address!= 5'd0)) // write if it is not the 0th register
20         begin
21             registers[write_address] <= write_data;
22         end
23     end
24
25     // hard wire the 0th register to zero
26     assign reg_out_1 = (read_address_1 == 5'd0) ? 32'd0 : registers[read_address_1];
27     assign reg_out_2 = (read_address_2 == 5'd0) ? 32'd0 : registers[read_address_2];
28
29 endmodule
```

4.7 Sign Extender

≡ sign_extender.v

```
1  module sign_extender (  
2      input [15:0] in,  
3      output [31:0] out  
4  );  
5      assign out = {{16{in[15]}}, in};  
6  endmodule
```

4.8 Control Unit

≡ control_unit.v

```
1  module control_unit (
2      input [5:0] op_code,
3      output reg [1:0] register_destination, alu_op,
4      output reg jump, branch, memory_read, memory_write, memory_to_register, alu_source,
5      output reg reg_write, pc_control, memory_write_source, memory_read_source
6  );
7      always @(*) begin
8
9          // initialize everything to zero
10         register_destination = 2'b00;
11         alu_op = 2'b00;
12         jump = 1'b0;
13         branch = 1'b0;
14         memory_read = 1'b0;
15         memory_write = 1'b0;
16         memory_to_register = 1'b0;
17         alu_source = 1'b0;
18         reg_write = 1'b0;
19         pc_control = 1'b0;
20         memory_write_source = 1'b0;
21         memory_read_source = 1'b0;
22
23         case (op_code)
24
25             6'b000000: begin // all R-type instructions
26                 alu_op = 2'b10;
27                 reg_write = 1'b1;
28                 register_destination = 2'b01;
29             end
30
31             6'b100011: begin // lw instruction
32                 alu_source = 1'b1;
33                 memory_read = 1'b1;
34                 memory_to_register = 1'b1;
35                 reg_write = 1'b1;
36             end
37
38             6'b101011: begin // sw instruction
39                 memory_write = 1'b1;
40                 alu_source = 1'b1;
41             end
42
43             6'b000100: begin // branch instruction
44                 branch = 1'b1;
45                 alu_op = 2'b01;
46             end
```

4.8 Control Unit (Cont.)

```
48 6'b001000: begin // addi instruction
49 |   alu_source = 1'b1;
50 |   reg_write = 1'b1;
51 |   alu_op = 2'b00; // force add, it is 00 by default but i add it anyways to show that we treat addi as a normal add instruction
52 end
53
54 6'b001100: begin // andi instruction
55 |   alu_source = 1'b1;
56 |   alu_op = 2'b11;
57 |   reg_write = 1'b1;
58 end
59
60 6'b000010: begin // jump instruction
61 |   jump = 1'b1;
62 end
63
64 // custom instructions
65
66 6'b110000: begin // jump mem indirect instruction
67 |   alu_source = 1'b1;
68 |   memory_read = 1'b1;
69 |   alu_op = 2'b00; // force add
70 |   pc_control = 1'b1;
71 end
72
73 6'b110001: begin // store and increment instruction
74 |   alu_source = 1'b1;
75 |   register_destination = 2'b10;
76 |   reg_write = 1'b1;
77 |   memory_write = 1'b1;
78 end
79
80 6'b110010: begin // program mem copy instruction
81 |   alu_source = 1'b1;
82 |   pc_control = 1'b1;
83 |   memory_read = 1'b1;
84 |   memory_write = 1'b1;
85 |   memory_write_source = 1'b1;
86 |   memory_read_source = 1'b1;
87 |   end
88 endcase
89 end
90 endmodule
```

4.9 Hazard Detection Unit

hazard_detection_unit.v

```
1  module hazard_detection_unit (  
2      input [4:0] id_rs, id_rt, ex_rt,  
3      input mem_read,  
4      output reg hazard_flag, if_id_write_enable, pc_write_enable  
5  );  
6      always @(*) begin  
7          hazard_flag = 1'b0;  
8          if_id_write_enable = 1'b1;  
9          pc_write_enable = 1'b1;  
10  
11         if (mem_read && ( (id_rs == ex_rt) || (id_rt == ex_rt) ) ) begin  
12             hazard_flag = 1'b1;  
13             if_id_write_enable = 1'b0;  
14             pc_write_enable = 1'b0;  
15         end  
16     end  
17 end  
18 endmodule
```

4.10 ID EX Stage Register

```
id_ex_stage.v
1  module id_ex_stage (
2
3      //*****
4      //inputs
5      //*****
6
7      // system signals
8      input clk, rst,
9      input flush,
10
11     // data signals
12     input [31:0] pc_in, pc_plus_4_in, reg_file_out_1_in, reg_file_out_2_in, sign_extended_in,
13     input [4:0] reg_rs_address_in, reg_rt_address_in, reg_rd_address_in,
14     input [5:0] funct_in,
15
16     // control signals
17     input [1:0] register_destination_in, alu_op_in,
18     input branch_in, memory_read_in, memory_write_in, memory_to_register_in,
19     input alu_source_in, reg_write_in, pc_control_in, memory_write_source_in, memory_read_source_in,
20
21     //*****
22     // outputs
23     //*****
24
25     // data signals
26     output reg [31:0] pc_out, pc_plus_4_out, reg_file_out_1_out, reg_file_out_2_out, sign_extended_out,
27     output reg [4:0] reg_rs_address_out, reg_rt_address_out, reg_rd_address_out,
28     output reg [5:0] funct_out,
29
30     // control signals
31     output reg [1:0] register_destination_out, alu_op_out,
32     output reg branch_out, memory_read_out, memory_write_out, memory_to_register_out,
33     output reg alu_source_out, reg_write_out, pc_control_out, memory_write_source_out, memory_read_source_out
34 );
```


4.10 ID EX Stage Register (Cont.)

```
36      always @(posedge clk or posedge rst) begin
37          if (rst) begin
38              pc_out <= 32'd0;
39              pc_plus_4_out <= 32'd0;
40              reg_file_out_1_out <= 32'd0;
41              reg_file_out_2_out <= 32'd0;
42              sign_extended_out <= 32'd0;
43
44              reg_rs_address_out <= 5'd0;
45              reg_rt_address_out <= 5'd0;
46              reg_rd_address_out <= 5'd0;
47
48              funct_out <= 6'd0;
49
50              register_destination_out <= 2'd0;
51              alu_op_out <= 2'd0;
52
53              branch_out <= 1'd0;
54              memory_read_out <= 1'd0;
55              memory_write_out <= 1'd0;
56              memory_to_register_out <= 1'd0;
57              alu_source_out <= 1'd0;
58              reg_write_out <= 1'd0;
59              pc_control_out <= 1'd0;
60              memory_write_source_out <= 1'd0;
61              memory_read_source_out <= 1'd0;
62          end
        end
```

4.10 ID EX Stage Register (Cont.)

```
63      else if (flush) begin
64          pc_out <= 32'd0;
65          pc_plus_4_out <= 32'd0;
66          reg_file_out_1_out <= 32'd0;
67          reg_file_out_2_out <= 32'd0;
68          sign_extended_out <= 32'd0;
69
70          reg_rs_address_out <= 5'd0;
71          reg_rt_address_out <= 5'd0;
72          reg_rd_address_out <= 5'd0;
73
74          funct_out <= 6'd0;
75
76          register_destination_out <= 2'd0;
77          alu_op_out <= 2'd0;
78
79          branch_out <= 1'd0;
80          memory_read_out <= 1'd0;
81          memory_write_out <= 1'd0;
82          memory_to_register_out <= 1'd0;
83          alu_source_out <= 1'd0;
84          reg_write_out <= 1'd0;
85          pc_control_out <= 1'd0;
86          memory_write_source_out <= 1'd0;
87          memory_read_source_out <= 1'd0;
88      end
```

4.10 ID EX Stage Register (Cont.)

```
89     else begin
90         pc_out <= pc_in;
91         pc_plus_4_out <= pc_plus_4_in;
92         reg_file_out_1_out <= reg_file_out_1_in;
93         reg_file_out_2_out <= reg_file_out_2_in;
94         sign_extended_out <= sign_extended_in;
95
96         reg_rs_address_out <= reg_rs_address_in;
97         reg_rt_address_out <= reg_rt_address_in;
98         reg_rd_address_out <= reg_rd_address_in;
99
100        funct_out <= funct_in;
101
102        register_destination_out <= register_destination_in;
103        alu_op_out <= alu_op_in;
104
105        branch_out <= branch_in;
106        memory_read_out <= memory_read_in;
107        memory_write_out <= memory_write_in;
108        memory_to_register_out <= memory_to_register_in;
109        alu_source_out <= alu_source_in;
110        reg_write_out <= reg_write_in;
111        pc_control_out <= pc_control_in;
112        memory_write_source_out <= memory_write_source_in;
113        memory_read_source_out <= memory_read_source_in;
114    end
115
116 end
117
118 endmodule
```

4.11 ALU

alu.v

```
1  module alu (
2      input [31:0] input_1, input_2,
3      input [2:0] alu_control,
4      output reg [31:0] alu_result,
5      output zero_flag,
6      output reg overflow_flag
7  );
8      always @(*)
9      begin
10         overflow_flag = 1'b0; // default to zero and change to 1 if an overflow is detected
11         case (alu_control)
12             3'b000: begin
13                 alu_result = input_1+input_2; // add
14
15                 if ( (input_1[31] == input_2[31]) & (alu_result[31] != input_1[31]) )
16                     // if the inputs are +ve and the result is negative, then overflow, or visversa )
17                     begin
18                         overflow_flag = 1'b1;
19                     end
20             end
21             3'b001: begin
22                 alu_result = input_1-input_2; // sub
23
24                 if ( (input_1[31] != input_2[31]) & (alu_result[31] == input_2[31]) )
25                     // if +ve - -ve equal to -ve, then overflow
26                     // if -ve - +ve equal to +ve, then overflow
27                     begin
28                         overflow_flag = 1'b1;
29                     end
30             end
31             3'b010: alu_result = input_1&input_2; // and
32             3'b011: alu_result = input_1|input_2; // or
33             3'b100: alu_result = (input_1 < input_2)?32'd1:32'd0; // slt
34             default: alu_result = input_1+input_2; // default case is add to avoid latches
35         endcase
36     end
37
38     assign zero_flag = (alu_result == 32'd0) ? 1'b1 : 1'b0; // zero flag
39
40 endmodule
```

4.12 ALU Control Unit

alu_control_unit.v

```
1  module alu_control_unit (  
2      input [1:0] alu_op,  
3      input [5:0] funct,  
4      output reg [2:0] alu_control_out  
5  );  
6  
7      always @(*)  
8      begin  
9          case (alu_op)  
10             2'b00: alu_control_out = 3'b000; // add, force add for lw and sw instructions  
11             2'b01: alu_control_out = 3'b001; // sub, force sub for branch instruction  
12             2'b10:  
13                 begin  
14                     case (funct)  
15                         6'b100000: alu_control_out = 3'b000; // add  
16                         6'b100010: alu_control_out = 3'b001; // sub  
17                         6'b100100: alu_control_out = 3'b010; // and  
18                         6'b100101: alu_control_out = 3'b011; // or  
19                         6'b101010: alu_control_out = 3'b100; // slt  
20                         default: alu_control_out = 3'b000; // add  
21                     endcase  
22                 end  
23             2'b11: alu_control_out = 3'b010; //and, for andi instruction  
24             default: alu_control_out = 3'b000; // add  
25         endcase  
26     end  
27  
28 endmodule
```

4.13 MUX 4x1 32-Bits

```
1 module mux_4to1_32bits (  
2     input [31:0] input_1, input_2, input_3, input_4,  
3     input [1:0] select,  
4     output reg [31:0] mux_out  
5 );  
6  
7     always @(*) begin  
8         case (select)  
9             2'b00: mux_out = input_1; // default alu input  
10            2'b01: mux_out = input_2; // destination register of ex_mem stage  
11            2'b10: mux_out = input_3; // destination register of mem_wb stage  
12            2'b11: mux_out = input_4; // 32'd0 for if the destination register was $0  
13            default: mux_out = input_1; // default alu input  
14        endcase  
15    end  
16 endmodule
```

4.14 MUX 4x1 5-Bits

```
1 module mux_4to1_5bits (  
2     input [4:0] input_1, input_2, input_3, input_4,  
3     input [1:0] select,  
4     output reg [4:0] mux_out  
5 );  
6  
7     always @(*) begin  
8         case (select)  
9             2'b00: mux_out = input_1; // for I-type  
10            2'b01: mux_out = input_2; // for R-type  
11            2'b10: mux_out = input_3; // for swi (custom instruction)  
12            2'b11: mux_out = input_4;  
13            default: mux_out = input_2; // default will be like normal I-type  
14        endcase  
15    end  
16 endmodule
```

4.15 Forwarding Unit

forwarding_unit.v

```
1  module forwarding_unit (
2      input [4:0] destination_register_of_1st_previous_instruction,
3      input [4:0] destination_register_of_2nd_previous_instruction,
4      input [4:0] source_register_1, source_register_2,
5      input reg_write_1st_instruction, reg_write_2nd_instruction,
6
7      output reg [1:0] alu_input_1, alu_input_2
8  );
9
10     always @(*) begin
11         if (source_register_1 == 5'd0) begin
12             | alu_input_1 = 2'b11; // if source is $0 register then pass 32'd0
13         end
14         else if ((source_register_1 == destination_register_of_1st_previous_instruction) && reg_write_1st_instruction) begin
15             | alu_input_1 = 2'b01; // pass the value from ex_mem registe
16         end
17         else if ((source_register_1 == destination_register_of_2nd_previous_instruction) && reg_write_2nd_instruction) begin
18             | alu_input_1 = 2'b10; // pass the value from mem_wb registe
19         end
20         else alu_input_1 = 2'b00; // pass the degault value form the single cycle (read data 1)
21     end
22
23     always @(*) begin
24         if (source_register_2 == 5'd0) begin
25             | alu_input_2 = 2'b11; // if source is $0 register then pass 32'd0
26         end
27         else if ((source_register_2 == destination_register_of_1st_previous_instruction) && reg_write_1st_instruction) begin
28             | alu_input_2 = 2'b01; // pass the value from ex_mem registe
29         end
30         else if ((source_register_2 == destination_register_of_2nd_previous_instruction) && reg_write_2nd_instruction) begin
31             | alu_input_2 = 2'b10; // pass the value from mem_wb registe
32         end
33         else alu_input_2 = 2'b00; // pass the degault value form the single cycle (alu_source mux output)
34     end
35
36 endmodule
```

4.16 EX MEM Stage Register

id_ex_stage.v

```
1  module id_ex_stage (  
2  
3      //*****  
4      //inputs  
5      //*****  
6  
7      // system signals  
8      input clk, rst,  
9      input flush,  
10  
11     // data signals  
12     input [31:0] pc_in, pc_plus_4_in, reg_file_out_1_in, reg_file_out_2_in, sign_extended_in,  
13     input [4:0] reg_rs_address_in, reg_rt_address_in, reg_rd_address_in,  
14     input [5:0] funct_in,  
15  
16     // control signals  
17     input [1:0] register_destination_in, alu_op_in,  
18     input branch_in, memory_read_in, memory_write_in, memory_to_register_in,  
19     input alu_source_in, reg_write_in, pc_control_in, memory_write_source_in, memory_read_source_in,  
20  
21     //*****  
22     // outputs  
23     //*****  
24  
25     // data signals  
26     output reg [31:0] pc_out, pc_plus_4_out, reg_file_out_1_out, reg_file_out_2_out, sign_extended_out,  
27     output reg [4:0] reg_rs_address_out, reg_rt_address_out, reg_rd_address_out,  
28     output reg [5:0] funct_out,  
29  
30     // control signals  
31     output reg [1:0] register_destination_out, alu_op_out,  
32     output reg branch_out, memory_read_out, memory_write_out, memory_to_register_out,  
33     output reg alu_source_out, reg_write_out, pc_control_out, memory_write_source_out, memory_read_source_out  
34 );
```


4.16 EX MEM Stage Register (Cont.)

```
36     always @(posedge clk or posedge rst) begin
37         if (rst) begin
38             pc_out <= 32'd0;
39             pc_plus_4_out <= 32'd0;
40             reg_file_out_1_out <= 32'd0;
41             reg_file_out_2_out <= 32'd0;
42             sign_extended_out <= 32'd0;
43
44             reg_rs_address_out <= 5'd0;
45             reg_rt_address_out <= 5'd0;
46             reg_rd_address_out <= 5'd0;
47
48             funct_out <= 6'd0;
49
50             register_destination_out <= 2'd0;
51             alu_op_out <= 2'd0;
52
53             branch_out <= 1'd0;
54             memory_read_out <= 1'd0;
55             memory_write_out <= 1'd0;
56             memory_to_register_out <= 1'd0;
57             alu_source_out <= 1'd0;
58             reg_write_out <= 1'd0;
59             pc_control_out <= 1'd0;
60             memory_write_source_out <= 1'd0;
61             memory_read_source_out <= 1'd0;
62         end
end
```

4.16 EX MEM Stage Register (Cont.)

```
63     else if (flush) begin
64         pc_out <= 32'd0;
65         pc_plus_4_out <= 32'd0;
66         reg_file_out_1_out <= 32'd0;
67         reg_file_out_2_out <= 32'd0;
68         sign_extended_out <= 32'd0;
69
70         reg_rs_address_out <= 5'd0;
71         reg_rt_address_out <= 5'd0;
72         reg_rd_address_out <= 5'd0;
73
74         funct_out <= 6'd0;
75
76         register_destination_out <= 2'd0;
77         alu_op_out <= 2'd0;
78
79         branch_out <= 1'd0;
80         memory_read_out <= 1'd0;
81         memory_write_out <= 1'd0;
82         memory_to_register_out <= 1'd0;
83         alu_source_out <= 1'd0;
84         reg_write_out <= 1'd0;
85         pc_control_out <= 1'd0;
86         memory_write_source_out <= 1'd0;
87         memory_read_source_out <= 1'd0;
88     end
```

4.16 EX MEM Stage Register (Cont.)

```
89         else begin
90             pc_out <= pc_in;
91             pc_plus_4_out <= pc_plus_4_in;
92             reg_file_out_1_out <= reg_file_out_1_in;
93             reg_file_out_2_out <= reg_file_out_2_in;
94             sign_extended_out <= sign_extended_in;
95
96             reg_rs_address_out <= reg_rs_address_in;
97             reg_rt_address_out <= reg_rt_address_in;
98             reg_rd_address_out <= reg_rd_address_in;
99
100            funct_out <= funct_in;
101
102            register_destination_out <= register_destination_in;
103            alu_op_out <= alu_op_in;
104
105            branch_out <= branch_in;
106            memory_read_out <= memory_read_in;
107            memory_write_out <= memory_write_in;
108            memory_to_register_out <= memory_to_register_in;
109            alu_source_out <= alu_source_in;
110            reg_write_out <= reg_write_in;
111            pc_control_out <= pc_control_in;
112            memory_write_source_out <= memory_write_source_in;
113            memory_read_source_out <= memory_read_source_in;
114        end
115    end
116 end
117
118 endmodule
```

4.17 Data Memory

```
1 module data_memory (
2     input memory_read, memory_write, clk,
3     input [31:0] read_address, write_address, write_data,
4     output reg [31:0] output_data
5 );
6
7 wire [31:0] actual_read_address, actual_write_address;
8
9 // as each word (register) holds 4 bytes
10 // in other words, MIPS is byte aligned and each word is 4 bytes, so address if the alu result is 8, then this is the 2nd register and not the 8th
11 assign actual_read_address = read_address >> 2;
12 assign actual_write_address = write_address >> 2;
13
14 reg [31:0] data_memory_registers [0:1023];
15
16 initial // load "data.hex" into the data memory
17 begin
18     $readmemh("data.hex", data_memory_registers );
19 end
20
21 always @(*) begin
22
23     output_data = 32'd0; // default value to avoid latches
24
25     if (memory_read) begin
26         if (actual_read_address > 32'd1023) begin
27             output_data = data_memory_registers[1023];
28         end
29         else begin
30             output_data = data_memory_registers[actual_read_address];
31         end
32     end
33 end
34
35 always @(posedge clk) begin // write is synchronous to avoid potential errors, as we must make sure that the write address is ready and stable before actually write in it
36     if (memory_write) begin
37         if (actual_write_address > 32'd1023) begin
38             data_memory_registers[1023] <= write_data;
39         end
40         else begin
41             data_memory_registers[actual_write_address] <= write_data;
42         end
43     end
44 end
45
46 endmodule
```

4.18 MEM WB Stage Register

```
mem_wb_stage.v
1  module mem_wb_stage (
2
3      //*****
4      //inputs
5      //*****
6
7      input clk, rst,
8
9      input [31:0] pc_in,
10
11     // data signals
12     input [31:0] memory_data_in, alu_result_in,
13     input [4:0] register_destination_in,
14
15     // control signals
16     input memory_to_register_in, reg_write_in,
17     input overflow_flag_in,
18
19     //*****
20     //outputs
21     //*****
22
23     output reg [31:0] pc_out,
24
25     // data signals
26     output reg [31:0] memory_data_out, alu_result_out,
27     output reg [4:0] register_destination_out,
28
29     // control signals
30     output reg memory_to_register_out, reg_write_out,
31     output reg overflow_flag_out
32 );
```

4.18 MEM WB Stage Register (Cont.)

```
34  always @(posedge clk or posedge rst) begin
35      if (rst) begin
36          pc_out <= 32'd0;
37
38          memory_data_out <= 32'd0;
39          alu_result_out <= 32'd0;
40
41          register_destination_out <= 5'd0;
42
43          memory_to_register_out <= 1'd0;
44          reg_write_out <= 1'd0;
45
46          overflow_flag_out <= 1'd0;
47      end
48      else begin
49          pc_out <= pc_in;
50
51          memory_data_out <= memory_data_in;
52          alu_result_out <= alu_result_in;
53
54          register_destination_out <= register_destination_in;
55
56          memory_to_register_out <= memory_to_register_in;
57          reg_write_out <= reg_write_in;
58
59          overflow_flag_out <= overflow_flag_in;
60      end
61  end
62
63  endmodule
```

4.19 Top Module

top_module.v

```
1  module top_module (  
2      input clk, rst  
3  );  
4  
5      //*****  
6      //wires declaration  
7      //*****  
8  
9      //*****  
10     //if stage  
11     //*****  
12  
13     wire [31:0] if_current_pc, if_instruction, if_current_pc_plus_4;  
14  
15     wire [31:0] if_branch_mux_output, if_jump_mux_output, if_pmc_mux_output;  
16  
17     //*****  
18     //id stage  
19     //*****  
20  
21     wire [31:0] id_instruction, id_pc, id_pc_plus_4;  
22  
23     // control signals  
24     wire [1:0] id_register_destination, id_alu_op;  
25     wire id_jump, id_branch, id_memory_read, id_memory_write, id_memory_to_register, id_alu_source;  
26     wire id_reg_write, id_pc_control, id_memory_write_source, id_memory_read_source;  
27  
28     // register file signals  
29     wire [31:0] id_register_out_1, id_register_out_2;  
30  
31     // sign extender signal  
32     wire [31:0] id_sign_extended;  
33  
34     // hazard detection signals  
35     wire id_hazard_flag, id_pc_write_enable, if_id_write_enable;  
36  
37     // jump signals  
38     wire [31:0] id_jump_address;  
39     wire [27:0] id_jump_imm_shifted_by_2;
```

4.19 Top Module (Cont.)

```
41 //*****
42 //ex stage
43 //*****
44
45 wire [31:0] ex_pc;
46
47 // MUXs inputs
48 wire [31:0] ex_mux_1_input_1, ex_mux_1_input_2, ex_mux_1_input_3, ex_mux_1_input_4;
49 wire [31:0] ex_mux_2_input_1, ex_mux_2_input_2, ex_mux_2_input_3, ex_mux_2_input_4;
50 wire [31:0] ex_alu_source_mux_input_1, ex_alu_source_mux_input_2;
51
52 // MUXs outputs
53 wire [31:0] ex_mux_1_output, ex_mux_2_output, ex_alu_source_mux_output;
54
55 // MUXs control signals
56 wire ex_alu_source;
57 wire [1:0] ex_alu_input_1_select, ex_alu_input_2_select;
58
59 // alu control unit signals
60 wire [1:0] ex_alu_op;
61 wire [2:0] ex_alu_control;
62 wire [5:0] ex_func;
63
64 // register addresses
65 wire [4:0] ex_rt_address, ex_rd_address, ex_rs_address;
66 wire [4:0] ex_destination_register;
67
68 // alu signals
69 wire [31:0] ex_alu_result;
70 wire ex_zero_flag, ex_overflow_flag;
71
72 // branch signals
73 wire [31:0] ex_pc_plus_4, ex_imm, ex_imm_shifted_by_2;
74 wire [31:0] ex_branch_address;
75
76 // control signals
77 wire [1:0] ex_register_destination;
78 wire ex_branch, ex_memory_read, ex_memory_write, ex_memory_to_register;
79 wire ex_reg_write, ex_pc_control, ex_memory_write_source, ex_memory_read_source;
```


4.19 Top Module (Cont.)

```
81 //*****
82 //mem stage
83 //*****
84
85 wire [31:0] mem_pc;
86
87 // memory MUXs signals
88 wire [31:0] mem_alu_result, mem_register_file_output_2, mem_pc_plus_4;
89
90 // control signals
91 wire mem_branch_control;
92
93 // memory singals
94 wire [31:0] mem_memory_read_address, mem_memory_write_data;
95 wire [31:0] mem_memory_in_data, mem_memory_out_data;
96
97 // branch address
98 wire [31:0] mem_branch_address;
99
100 // control signals
101 wire mem_branch, mem_memory_read, mem_memory_write, mem_memory_to_register;
102 wire mem_reg_write, mem_pc_control, mem_memory_write_source, mem_memory_read_source;
103
104 wire [4:0] mem_destination_register;
105 wire mem_zero_flag, mem_overflow_flag;
106
107 //*****
108 //wb stage
109 //*****
110
111 wire [31:0] wb_pc;
112
113 // memory to register mux signals
114 wire [31:0] wb_memory_data, wb_alu_result, wb_register_file_data_wrtie;
115
116 // control signals
117 wire wb_memory_to_register;
118 wire wb_reg_write;
119 wire [4:0] wb_register_destination;
120
121 wire wb_overflow_flag;
```

4.19 Top Module (Cont.)

```
123 //*****
124 //some extra assigns
125 //*****
126
127 // jump address
128 assign id_jump_imm_shifted_by_2 = {id_instruction[25:0], 2'b00};
129 assign id_jump_address = {id_pc_plus_4[31:28], id_jump_imm_shifted_by_2};
130
131 // branch address
132 assign ex_imm_shifted_by_2 = {ex_alu_source_mux_input_2[29:0], 2'b00};
133
134 // 4th input for alu
135 assign ex_mux_1_input_4 = 32'd0;
136 assign ex_mux_2_input_4 = 32'd0;
137
138 // branch control
139 assign mem_branch_control = mem_branch & mem_zero_flag;
140
141 // flush signals
142 assign mem_stage_flush_trigger = mem_branch_control | mem_pc_control;
143 assign if_id_flush = id_jump | mem_stage_flush_trigger;
144 assign id_ex_flush = mem_stage_flush_trigger | id_hazard_flag;
```

4.19 Top Module (Cont.)

```
147     mux_2to1_32bits branch_mux (  
148         .input_1(if_current_pc_plus_4), .input_2(mem_branch_address),  
149         .select(mem_branch_control),  
150         .mux_out(if_branch_mux_output)  
151     );  
152  
153     mux_2to1_32bits jump_mux (  
154         .input_1(if_branch_mux_output), .input_2(id_jump_address),  
155         .select(id_jump),  
156         .mux_out(if_jump_mux_output)  
157     );  
158  
159     mux_2to1_32bits pmc_mux (  
160         .input_1(if_jump_mux_output), .input_2(mem_memory_out_data),  
161         .select(mem_pc_control),  
162         .mux_out(if_pmc_mux_output)  
163     );  
164  
165     program_counter program_counter_module (  
166         .next_pc(if_pmc_mux_output),  
167         .clk(clk), .rst(rst), .overflow_flag(wb_overflow_flag), .write_enable(id_pc_write_enable),  
168         .current_pc(if_current_pc)  
169     );  
170  
171     instruction_memory instruction_memory_module (  
172         .pc(if_current_pc),  
173         .instruction(if_instruction)  
174     );  
175  
176     adder_pc_adder_module (  
177         .input_1(32'd4), .input_2(if_current_pc),  
178         .adder_output(if_current_pc_plus_4)  
179     );  
180  
181     if_id_stage if_id_stage_register (  
182         .clk(clk), .rst(rst),  
183         .write_enable(if_id_write_enable), .flush(if_id_flush),  
184         .instruction_in(if_instruction), .pc_in(if_current_pc), .pc_plus_4_in(if_current_pc_plus_4),  
185         .instruction_out(id_instruction), .pc_out(id_pc), .pc_plus_4_out(id_pc_plus_4)  
186     );
```

4.19 Top Module (Cont.)

```
188 register_file register_file_module (  
189     .read_address_1(id_instruction[25:21]), .read_address_2(id_instruction[20:16]),  
190     .write_address(wb_register_destination), .write_data(wb_register_file_data_wrtie),  
191     .reg_write(wb_reg_write), .clk(clk), .rst(rst),  
192     .reg_out_1(id_register_out_1), .reg_out_2(id_register_out_2)  
193 );  
194  
195 sign_extender sign_extender_module (  
196     .in(id_instruction[15:0]), .out(id_sign_extended)  
197 );  
198  
199 control_unit control_unit_module (  
200     .op_code(id_instruction[31:26]),  
201     .register_destination(id_register_destination), .alu_op(id_alu_op),  
202     .jump(id_jump), .branch(id_branch), .memory_read(id_memory_read),  
203     .memory_write(id_memory_write), .memory_to_register(id_memory_to_register),  
204     .alu_source(id_alu_source), .reg_write(id_reg_write), .pc_control(id_pc_control),  
205     .memory_write_source(id_memory_write_source), .memory_read_source(id_memory_read_source)  
206 );  
207  
208 hazard_detection_unit hazard_detection_unit_module (  
209     .id_rs(id_instruction[25:21]), .id_rt(id_instruction[20:16]), .ex_rt(ex_rt_address),  
210     .mem_read(ex_memory_read),  
211     .hazard_flag(id_hazard_flag), .if_id_write_enable(if_id_write_enable), .pc_write_enable(id_pc_write_enable)  
212 );
```

4.19 Top Module (Cont.)

```
214 id_ex_stage id_ex_stage_register (
215     //*****
216     //inputs
217     //*****
218
219     // system signals
220     .clk(clk), .rst(rst),
221     .flush(id_ex_flush),
222
223     // data signals
224     .pc_in(id_pc), .pc_plus_4_in(id_pc_plus_4), .reg_file_out_1_in(id_register_out_1),
225     .reg_file_out_2_in(id_register_out_2), .sign_extended_in(id_sign_extended),
226     .reg_rs_address_in(id_instruction[25:21]), .reg_rt_address_in(id_instruction[20:16]),
227     .reg_rd_address_in(id_instruction[15:11]), .funct_in(id_instruction[5:0]),
228
229     // control signals
230     .register_destination_in(id_register_destination), .alu_op_in(id_alu_op),
231     .branch_in(id_branch), .memory_read_in(id_memory_read),
232     .memory_write_in(id_memory_write), .memory_to_register_in(id_memory_to_register),
233     .alu_source_in(id_alu_source), .reg_write_in(id_reg_write), .pc_control_in(id_pc_control),
234     .memory_write_source_in(id_memory_write_source), .memory_read_source_in(id_memory_read_source),
235
236     //*****
237     // outputs
238     //*****
239
240     // data signals
241     .pc_out(ex_pc), .pc_plus_4_out(ex_pc_plus_4), .reg_file_out_1_out(ex_mux_1_input_1),
242     .reg_file_out_2_out(ex_alu_source_mux_input_1), .sign_extended_out(ex_alu_source_mux_input_2),
243     .reg_rs_address_out(ex_rs_address), .reg_rt_address_out(ex_rt_address),
244     .reg_rd_address_out(ex_rd_address), .funct_out(ex_funct),
245
246     // control signals
247     .register_destination_out(ex_register_destination), .alu_op_out(ex_alu_op),
248     .branch_out(ex_branch), .memory_read_out(ex_memory_read),
249     .memory_write_out(ex_memory_write), .memory_to_register_out(ex_memory_to_register),
250     .alu_source_out(ex_alu_source), .reg_write_out(ex_reg_write), .pc_control_out(ex_pc_control),
251     .memory_write_source_out(ex_memory_write_source), .memory_read_source_out(ex_memory_read_source)
252 );
```

4.19 Top Module (Cont.)

```
254   adder_branch_adder_module (  
255       .input_1(ex_pc_plus_4), .input_2(ex_imm_shifted_by_2),  
256       .adder_output(ex_branch_address)  
257   );  
258  
259   mux_4to1_32bits alu_input_1_mux (  
260       .input_1(ex_mux_1_input_1), .input_2(ex_mux_1_input_2),  
261       .input_3(ex_mux_1_input_3), .input_4(ex_mux_1_input_4),  
262       .select(ex_alu_input_1_select),  
263       .mux_out(ex_mux_1_output)  
264   );  
265  
266   mux_2to1_32bits alu_source_mux (  
267       .input_1(ex_alu_source_mux_input_1), .input_2(ex_alu_source_mux_input_2),  
268       .select(ex_alu_source),  
269       .mux_out(ex_mux_2_input_1)  
270   );  
271  
272   mux_4to1_32bits alu_input_2_mux (  
273       .input_1(ex_mux_2_input_1), .input_2(ex_mux_2_input_2),  
274       .input_3(ex_mux_2_input_3), .input_4(ex_mux_2_input_4),  
275       .select(ex_alu_input_2_select),  
276       .mux_out(ex_mux_2_output)  
277   );  
278  
279   alu alu_module (  
280       .input_1(ex_mux_1_output), .input_2(ex_mux_2_output),  
281       .alu_control(ex_alu_control),  
282       .alu_result(ex_alu_result),  
283       .zero_flag(ex_zero_flag),  
284       .overflow_flag(ex_overflow_flag)  
285   );  
286  
287   alu_control_unit alu_control_unit_module (  
288       .alu_op(ex_alu_op),  
289       .funct(ex_funct),  
290       .alu_control_out(ex_alu_control)  
291   );  
292  
293   mux_4to1_5bits destination_register_mux (  
294       .input_1(ex_rt_address), .input_2(ex_rd_address),  
295       .input_3(ex_rs_address), .input_4(5'd0),  
296       .select(ex_register_destination),  
297       .mux_out(ex_destination_register)  
298   );
```

4.19 Top Module (Cont.)

```
300 forwarding_unit forwarding_unit_module (
301     .destination_register_of_1st_previous_instruction(mem_destination_register),
302     .destination_register_of_2nd_previous_instruction(wb_register_destination),
303     .source_register_1(ex_rs_address), .source_register_2(ex_rt_address),
304     .reg_write_1st_instruction(mem_reg_write), .reg_write_2nd_instruction(wb_reg_write),
305
306     .alu_input_1(ex_alu_input_1_select), .alu_input_2(ex_alu_input_2_select)
307 );
308
309 ex_mem_stage ex_mem_stage_register (
310     //*****
311     //inputs
312     //*****
313
314     .clk(clk), .rst(rst), .flush(mem_stage_flush_trigger),
315     .branch_target_in(ex_branch_address), .pc_in(ex_pc), .pc_plus_4_in(ex_pc_plus_4),
316     .alu_result_in(ex_alu_result), .reg_file_out_2_in(ex_alu_source_mux_input_1),
317     .register_destination_in(ex_register_destination),
318     .zero_flag_in(ex_zero_flag), .overflow_flag_in(ex_overflow_flag),
319
320     // control signals
321     .branch_in(ex_branch), .memory_read_in(ex_memory_read),
322     .memory_write_in(ex_memory_write), .memory_to_register_in(ex_memory_to_register),
323     .reg_write_in(ex_reg_write), .pc_control_in(ex_pc_control),
324     .memory_write_source_in(ex_memory_write_source), .memory_read_source_in(ex_memory_read_source),
325
326     //*****
327     // outputs
328     //*****
329
330     .branch_target_out(mem_branch_address), .pc_out(mem_pc), .pc_plus_4_out(mem_pc_plus_4),
331     .alu_result_out(mem_alu_result), .reg_file_out_2_out(mem_register_file_output_2),
332     .register_destination_out(mem_destination_register),
333     .zero_flag_out(mem_zero_flag), .overflow_flag_out(mem_overflow_flag),
334
335     // control signals
336     .branch_out(mem_branch), .memory_read_out(mem_memory_read),
337     .memory_write_out(mem_memory_write), .memory_to_register_out(mem_memory_to_register),
338     .reg_write_out(mem_reg_write), .pc_control_out(mem_pc_control),
339     .memory_write_source_out(mem_memory_write_source), .memory_read_source_out(mem_memory_read_source)
340 );
```

4.19 Top Module (Cont.)

```
342     mux_2to1_32bits memory_read_source_mux (  
343         .input_1(mem_alu_result), .input_2(mem_register_file_output_2),  
344         .select(mem_memory_read_source),  
345         .mux_out(mem_memory_read_address)  
346     );  
347  
348     mux_2to1_32bits memory_data_write_source_mux (  
349         .input_1(mem_register_file_output_2), .input_2(mem_pc_plus_4),  
350         .select(mem_memory_write_source),  
351         .mux_out(mem_memory_write_data)  
352     );  
353  
354     data_memory data_memory_module (  
355         .memory_read(mem_memory_read), .memory_write(mem_memory_write), .clk(clk),  
356         .read_address(mem_memory_read_address), .write_address(mem_alu_result),  
357         .write_data(mem_memory_write_data),  
358         .output_data(mem_memory_out_data)  
359     );
```


4.19 Top Module (Cont.)

```
361 mem_wb_stage mem_wb_stage_register (
362     //*****
363     //inputs
364     //*****
365
366     .clk(clk), .rst(rst),
367
368     .pc_in(mem_pc),
369
370     // data signals
371     .memory_data_in(mem_memory_out_data), .alu_result_in(mem_alu_result),
372     .register_destination_in(mem_destination_register),
373
374     // control signals
375     .memory_to_register_in(mem_memory_to_register), .reg_write_in(mem_reg_write),
376     .overflow_flag_in(mem_overflow_flag),
377
378     //*****
379     //outputs
380     //*****
381
382     .pc_out(wb_pc),
383
384     // data signals
385     .memory_data_out(wb_memory_data), .alu_result_out(wb_alu_result),
386     .register_destination_out(wb_register_destination),
387
388     // control signals
389     .memory_to_register_out(wb_memory_to_register), .reg_write_out(wb_reg_write),
390     .overflow_flag_out(wb_overflow_flag)
391 );
392
393 mux_2to1_32bits data_to_register_mux (
394     .input_1(wb_alu_result), .input_2(wb_memory_data),
395     .select(wb_memory_to_register),
396     .mux_out(wb_register_file_data_wrtie)
397 );
```

4.19 Top Module (Cont.)

```
399 // overflow monitoring block
400 always @(posedge clk) begin
401     if (wb_overflow_flag) begin
402         $display("-----");
403         $display("CRITICAL ERROR: Arithmetic Overflow Detected!");
404         $display("Processor Halted at Faulting PC = %h", wb_pc);
405         $display("-----");
406         $stop;
407     end
408 end
409
410 endmodule
```

5.0 SYNTHESIS AND IMPLEMENTATION

The RTL design was synthesized and implemented using Xilinx Vivado 2023. The target hardware was the **Xilinx Spartan-7 FPGA (xc7s50csga324-1)**. To accurately benchmark the total gate-level logic utilized by the architecture, a compiler directive (* dont_touch = "true" *) was applied to all submodules. This forced the synthesis engine to map the Data Memory directly to logic slices (Flip-Flops) rather than dedicated Block RAM (BRAM).

Implementation Results:

- **Slice LUTs (Look-Up Tables):** 11,333
- **Slice Registers (Flip-Flops):** 34,366
- **Worst Negative Slack (WNS):** +0.540 ns
- **Target Clock Constraint:** 10.000 ns (100 MHz)
- **Calculated Maximum Frequency (F_{max}):** 105.7 MHz

The timing report confirms that all user-specified timing constraints were met with zero setup or hold violations.

 


Figure 6: Elaboration schematic (post-elaboration netlist view).

 


Figure 7: Elaboration schematic (Expanded View).

 


Figure 8: Synthesis schematic.

 


Figure 9: Synthesis schematic (Expanded).

Name	1	Slice LUTs	Slice Registers	F7 Muxes	F8 Muxes	Bonded IOB	BUFGCTRL
✓ N top_module		11333	34366	4608	2176	2	1
I alu_module (alu)		153	0	0	0	0	0
I data_memory_module (data_memory)		10046	32768	4352	2176	0	0
I ex_mem_stage_register (ex_mem_stage)		90	180	0	0	0	0
I id_ex_stage_register (id_ex_stage)		97	194	0	0	0	0
I if_id_stage_register (if_id_stage)		49	96	0	0	0	0
I mem_wb_stage_register (mem_wb_stage)		0	104	0	0	0	0
I register_file_module (register_file)		607	992	256	0	0	0

Figure 10: Synthesis resource utilization (LUTs, FFs, BRAM, DSP slices).

Design Timing Summary

Setup	Hold	Pulse Width
Worst Negative Slack (WNS) 0.540 ns	Worst Hold Slack (WHS) 0.154 ns	Worst Pulse Width Slack (WPWS) 4.500 ns
Total Negative Slack (TNS) 0.000 ns	Total Hold Slack (THS) 0.000 ns	Total Pulse Width Negative Slack (TPWS) 0.000 ns
Number of Failing Endpoints 0	Number of Failing Endpoints 0	Number of Failing Endpoints 0
Total Number of Endpoints 68227	Total Number of Endpoints 68227	Total Number of Endpoints 34367
All user specified timing constraints are met.		

Figure 11: Synthesis timing report excerpt (critical path and Fmax)

 


Figure 12: Device view on the target FPGA.

 


Figure 13: Zoomed in Device View.

6.0 CONCLUSION

Phase 1 of the MIPS processor project was highly successful. The RTL architecture correctly implements a 5-stage pipeline with robust hardware-level hazard resolution. Synthesizing the design proved that the Verilog code is not just simulation-ready, but physically realizable, achieving a stable clock speed of over 100 MHz on a modern Spartan-7 architecture. With the RTL hardware fully implemented and benchmarked, the project is now prepared for Phase 2: rigorous functional verification utilizing a SystemVerilog UVM testbench.

7.0 References

- [1] Technical University of Cluj-Napoca, "Lab 10," [Online]. Available: <https://mihai.utcluj.ro/wp-content/uploads/ca/labs/Lab10.pdf>. (Accessed: Feb. 22, 2026).
- [2] Stack Overflow, "MIPS pipeline CPU architecture," [Online]. Available: <https://stackoverflow.com/questions/44331059/mips-pipeline-cpu-architecture>. (Accessed: Feb. 22, 2026).
- [3] D. A. Patterson and J. L. Hennessy, *Computer Organization and Design: The Hardware/Software Interface*, 5th ed. San Francisco, CA, USA: Morgan Kaufmann, 2013.
- [4] Xilinx, Inc., *Vivado Design Suite User Guide: Synthesis*, UG901, San Jose, CA, USA.
- [5] Xilinx, Inc., *Vivado Design Suite User Guide: Using Constraints*, UG903, San Jose, CA, USA.